

# Physics 3B Week 8: Current and Direct Current Circuits

i

Name: Andrea Silvestri ID#: \_\_\_\_\_

TA: Andrea Silvestri


Date: February 27, 2008

Day: Wednesday


Hour: 8:00 - 12:55
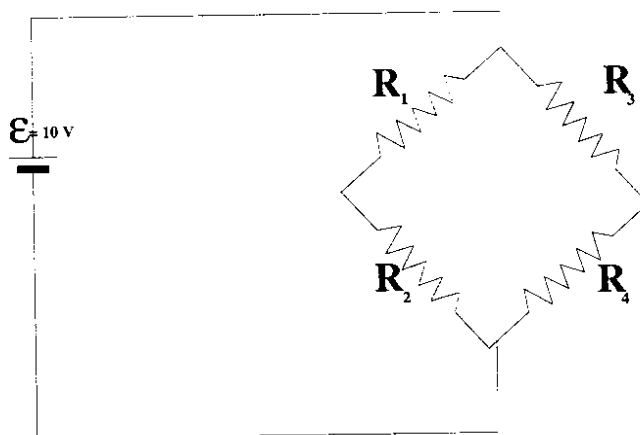
## 1. Problem 1

A  $\mathcal{E} = 10$  Volt battery is connected across four resistors. (a) Find the voltage drop across each resistor. (b) Find the current through each resistor. The four resistors have resistance: ( $R_1 = 1\Omega$ ,  $R_2 = 4\Omega$ ,  $R_3 = 8\Omega$ ,  $R_4 = 2\Omega$ .)




the circuit looks like this:

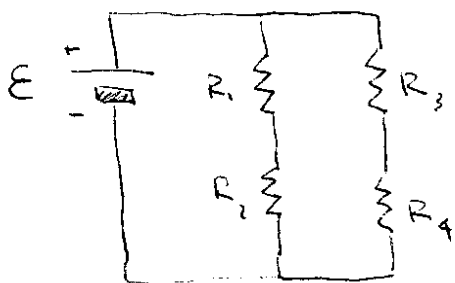


Resistors in series:  $R_L = R_1 + R_2$  (Left)

$R_R = R_3 + R_4$  (Right)

Resistors in parallel:

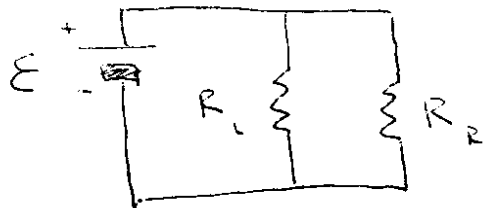
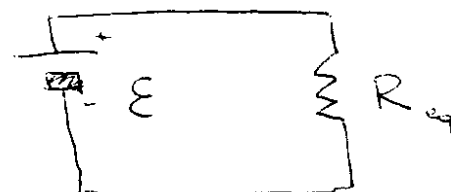
$$\frac{1}{R_{eq}} = \frac{1}{R_L} + \frac{1}{R_R}$$



$$R_L = 1\Omega + 4\Omega = 5\Omega;$$

$$\frac{1}{R_{eq}} = \frac{1}{5\Omega} + \frac{1}{10\Omega} = \frac{3}{10} \frac{1}{\Omega} \Rightarrow R_{eq} = \frac{10}{3}\Omega.$$

$$R_R = 8\Omega + 2\Omega = 10\Omega;$$

the total current:

$$I R_{eq} = \Delta V = \mathcal{E} = 10 \text{ V}; \Rightarrow I = \frac{\Delta V}{R_{eq}} = \frac{10 \text{ V}}{10/3 \Omega} = 3 \text{ A}$$

the individual currents:

$$I_L = \frac{\Delta V}{R_L} = \frac{10}{5} = 2 \text{ A}; \quad I_R = \frac{\Delta V}{R_R} = \frac{10}{10} = 1 \text{ A};$$

Since  $R_1$  and  $R_2$  in series  $\Rightarrow I_L = I_1 = I_2 = 2 \text{ A};$   $I_R = I_3 = I_4 = 1 \text{ A}$   
 $R_3$  "  $R_4$  in series

$$\Delta V_1 = I_1 R_1 = 2 \cdot 1 = 2 \text{ V} \quad \Delta V_3 = I_3 R_3 = 1 \cdot 8 = 8 \text{ V}$$

$$\Delta V_2 = I_2 R_2 = 2 \cdot 4 = 8 \text{ V} \quad \Delta V_4 = I_4 R_4 = 1 \cdot 2 = 2 \text{ V}$$



## 2. Problem 2

Vector  $\mathbf{A} = -2 \hat{\mathbf{j}}$  and vector  $\mathbf{B} = 3 \hat{\mathbf{k}}$ , calculate magnitude and direction of  $\mathbf{C} = \mathbf{A} \times \mathbf{B}$ , and draw the vectors in a Cartesian coordinate system, labeling all vectors ( $\mathbf{A}$ ,  $\mathbf{B}$ , and  $\mathbf{C}$ ).

ii
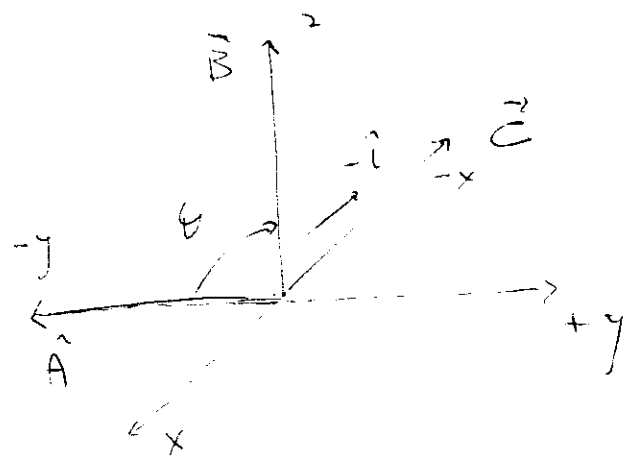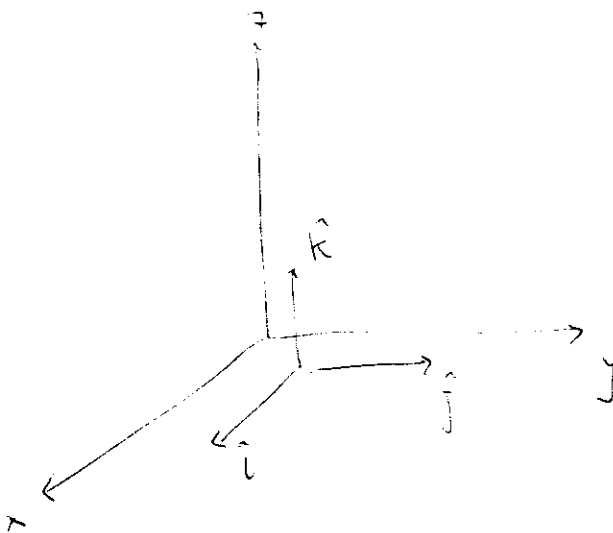
## 2. Problem 2

Vector  $\mathbf{A} = -2\hat{j}$  and vector  $\mathbf{B} = 3\hat{k}$ , calculate magnitude and direction of  $\mathbf{C} = \mathbf{A} \times \mathbf{B}$ , and draw the vectors in a Cartesian coordinate system, labeling all vectors ( $\mathbf{A}$ ,  $\mathbf{B}$ , and  $\mathbf{C}$ ).



$$|\vec{C}| = AB \sin \theta = 6 \sin 90^\circ = 6$$

$$\vec{C} = -6\hat{i}$$